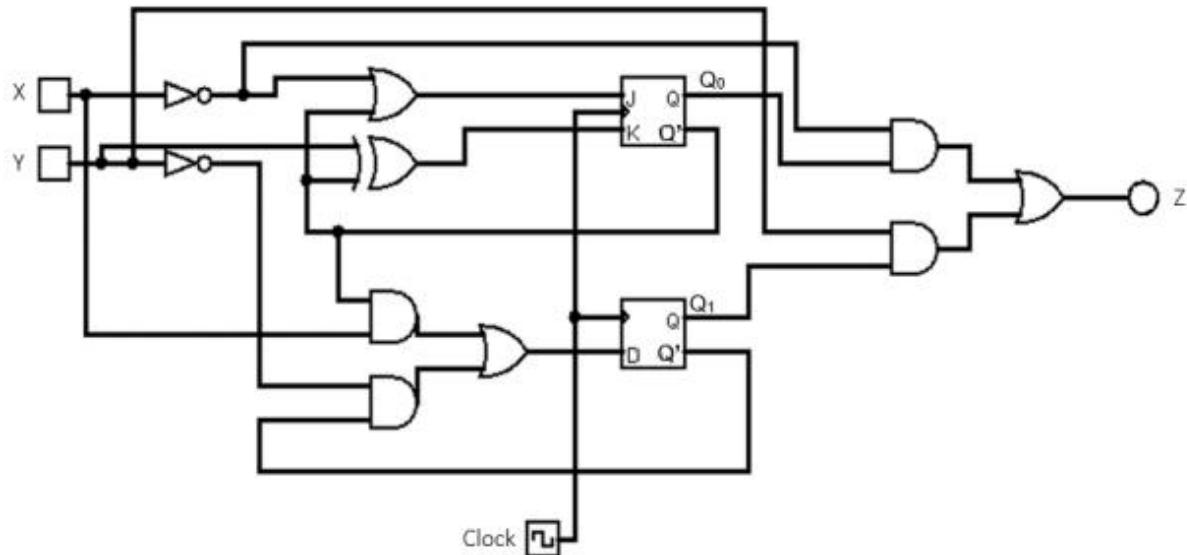


**Questions:**

A synchronous sequential circuit is given below:



1. Determine the type of this circuit: Mealy or Moore. Provide an explanation for your choice.

a. The inputs, and the current state determine the output of the function. This means it is a Mealy Model sequential circuit. If the output depended only on the current state, this would be a Moore model.

2. Find the simplest possible expressions for the functions that drive the  $J_0$ ,  $K_0$ , and  $D_1$  inputs of the flip-flops.

$$J_0 = ?$$

$$K_0 = ?$$

$$D_1 = ?$$

Present a detailed derivation for each expression.

b.  $J_0 = X' + Q_0'$

$$K_0 = Y \oplus Q_0' = Y \cdot Q_0 + Y' \cdot Q_0'$$

$$D_1 = Q_0' \cdot X + Q_1' \cdot Y'$$

3. Determine the simplest possible expressions for the next states  $Q_0^+$  and  $Q_1^+$  (using  $Q_0$  for the J-K flip-flop and  $Q_1$  for the D flip-flop) and the expression for the output Z.

$$Q_0^+ = ?$$

$$Q_1^+ = ?$$

$$Z = ?$$

c.

$$Q_0^+ = J_0 \cdot Q_0' + K_0' \cdot Q_0 \text{ (J-K FF characteristic function)}$$

$$Q_0^+ = (X' + Q_0') \cdot Q_0' + (Y' + Q_0') \cdot (Y + Q_0) \cdot Q_0$$

$$Q_0^+ = X' \cdot Q_0' + Q_0' + (Y' \cdot Y + Y' \cdot Q_0 + Q_0' \cdot Y + Q_0' \cdot Q_0) \cdot Q_0$$

$$Q_0^+ = Q_0' + (Y' \cdot Q_0 \cdot Q_0 + Q_0' \cdot Y \cdot Q_0)$$

$$Q_0^+ = Q_0' + Y' \cdot Q_0$$

$$Q_0^+ = Q_0' + Y' \text{ (minimization)}$$

$$Q_1^+ = D_1$$

$$Q_1^+ = Q_0' \cdot X + Q_1' \cdot Y'$$

$$Z = Q_0 \cdot X' + Q_1 \cdot Y$$

4. Create the state/output table, detailing the relationships between states and corresponding outputs.

d.

$Q_1^+ Q_0^+, Z$

XY Q <sub>1</sub> Q <sub>0</sub>	XY			
	00	01	10	11
00	11,0	01,0	11,0	11,0
01	11,1	00,1	11,0	00,0
10	01,0	01,1	11,0	11,1
11	01,1	00,1	01,0	00,1

$S^+, Z$

$\begin{array}{c} XY \\ S \end{array}$		00	01	10	11
A		D, 0	B, 0	D, 0	D, 0
B		D, 1	A, 1	D, 0	A, 0
C		B, 0	B, 1	D, 0	D, 1
D		B, 1	A, 1	B, 0	A, 1