

Week 1

Hamming distance: The hamming distance between two n -bit number determined by checking the same corresponding bits.

$1010 - 0100 \rightarrow \text{distance} : 3$

Decimal to binary: We divide the decimal number by 2 up to 0. After each operation the remainder is written to LSB to MSB.

$$15 \xrightarrow{1} 7 \xrightarrow{1} 3 \xrightarrow{1} 1 \xrightarrow{1} 0 : 1111$$

Negative numbers: First we take 1's complement of the unsigned number that corresponds to the negative one, then add 1 to this number. The whole operation is 2's complement.

$$\begin{array}{r} 0100 \rightarrow 1011 \\ (4) \quad + \underline{} 1 \\ \hline 1100 : -4 \end{array}$$

Addition (Unsigned):

$$\begin{array}{r} 01110101 : 117 \\ + 01100011 : 99 \\ \hline 10011000 : 216 \end{array}$$

Q → No carry

Addition (Signed):

1111 1111	: -1
+ 0000 0001	: 1
<hr/>	
0000 0000	: 0

Carry

$$\begin{array}{r} 11111111 : 255 \\ + 00000001 : 1 \\ \hline 1000000000 : 256 \end{array}$$

→ carry

we use the carry number
in unsigned numbers.

$$\begin{array}{r} 11111111 : -1 \\ + 11111111 : -1 \\ \hline 011111110 \\ \downarrow \text{carry} \end{array}$$

we ignore the carry numbers,
the next number determines
the sign.

Subtraction (Unsigned): $00000101 : 5$
 $\underline{-00000001 : 1}$ $\xrightarrow{2's \text{ comp.}}$

$00000101 : 5$
 $\underline{-11111111 : -1}$
 $(1)00000100 : 4$
 \rightarrow carry (no borrow)

There must be carry number when we carry out a subtraction operation with unsigned int, but we ignore the carry number.

00000001
 $\underline{-00000101}$ $\xrightarrow{2's \text{ comp.}}$ $00000001 : 1$
 $\underline{-11111011 : -5}$
 $011111100 \rightarrow$ cannot be represented

the carry number is "0", so we cannot represent this operation.

Overflow:

Addition \rightarrow pos. + pos. \rightarrow neg. | neg. + neg. \rightarrow pos.

Subtraction \rightarrow pos. - neg. \rightarrow neg. | neg. - pos. \rightarrow pos.

WEEK 2

Axioms

any $a, b \in B$

closure: $a+b \in B$, $a \cdot b \in B$
 commutative: $a+b = b+a$, $a \cdot b = b \cdot a$
 associative: $a+(b+c) = (a+b)+c$, $a \cdot (b \cdot c) = (a \cdot b) \cdot c$
 identity: $a+0 = a$, $a \cdot 1 = a$
 distributive: $a+(b \cdot c) = (a+b) \cdot (a+c)$, $a \cdot (b+c) = a \cdot b + a \cdot c$
 inverse: $a+\bar{a} = 1$, $a \cdot \bar{a} = 0$

• Duals of all proven theorems are also theorems.

Theorems

annihilator (dominance): $a+1 = 1$, $a \cdot 0 = 0$
 involution: $\bar{\bar{a}} = a$
 idempotency: $a+a = a$, $a \cdot a = a$
 absorption: $a+ab = a$, $a \cdot (a+b) = a$
 de morgan:

- $a \cdot b + \bar{a} \cdot c$ has 3 variables and 4 literals.

Disjunctive Normal Form (DNF): Sum of Products (SOP). OR of ANDs. $\rightarrow a \cdot b + c \cdot \bar{d} + \bar{e} \cdot f$

Conjunctive Normal Form (CNF): Product of Sums (POS). AND of ORs. $\rightarrow (a+b) \cdot (\bar{a}+c+d)$

Order Relation

$x_1: 1011$ If each component of x_1 is smaller than or equal to x_2 , $x_1 \leq x_2$. But there is no order relation between $x_2: 1101$ and x_2 .

If $E(x) \leq F(x)$ then $E(x)$ implies $F(x)$, $E(x) \Rightarrow F(x)$, $F(x)$ covers $E(x)$.

- $E + E \cdot F = E$
- $E \cdot (E + F) = E$

proof: $E \cdot 1 + E \cdot F \rightarrow E(1 + F) \rightarrow E$

- $E + \bar{E} \cdot F = E + F$
- $E \cdot (\bar{E} + F) = E \cdot F$

proof: $(E + \bar{E}) \cdot (E + F) \rightarrow 1 \cdot (E + F) \rightarrow E + F$

The Consensus Theorem (SOP Form)

$E_1(x_2, \dots, x_m), E_2(x_2, \dots, x_n)$

$F = x_1 \cdot E_1 + \bar{x}_1 \cdot E_2$ (x_1 is binary variable)

- $E_1 \cdot E_2$ is consensus term
- The consensus term is redundant and can be eliminated.

$x_1 E_1 + \bar{x}_1 E_2 + E_1 E_2 = x_1 E_1 + \bar{x}_1 E_2$

proof: $x_1 E_1 + \bar{x}_1 E_2 + E_1 E_2 (x_1 + \bar{x}_1) \rightarrow x_1 E_1 + \bar{x}_1 E_2 + x_1 E_1 E_2 + \bar{x}_1 E_1 E_2$ the pair ones can absorb the other one.

\downarrow
 $x_1 E_1 + \bar{x}_1 E_2$

The Consensus Theorem (POS Form)

$$F_1(x_1, \dots, x_n), F_2(x_1, \dots, x_m)$$

$$F = (x_1 + F_1) \cdot (\bar{x}_1 + F_2)$$

• $F_1 + F_2$ is consensus term

$$(x_1 + F_1) \cdot (\bar{x}_1 + F_2) \cdot (F_1 + F_2) = (x_1 + F_1)(\bar{x}_1 + F_2)$$

Boolean Functions

1) Basic Functions: Multiple inputs, single output.

• There are $2^{(2^n)}$ possible basic functions for n binary variables.

2) General Functions: Multiple inputs, multiple outputs.

3) Incompletely Specified Functions: Some of the outputs won't be generated. These outputs are don't care terms.

A	B	F
0	0	1
0	1	X
1	0	0
1	1	1

$\bar{A}B$ is don't care term.

X means it can be 0 or 1, we cannot demonstrate it.

Indexed Representations

Basic Function

Row Num.	Input	Output
	x_1, x_2	y
0	0 0	1
1	0 1	0
2	1 0	1
3	1 1	0

representation

$$y = f(x_1, x_2) = U_1(0, 2)$$

order is important
Set of 1-generating points

$$y = f(x_2, x_1) = U_1(0, 1)$$

$$y = f(x_1, x_2) = U_0(1, 3)$$

the row numbers of output 1

All three represents the same function.

Incompletely Specified Function

N	x_1	x_2	y_1	y_2
0	0	0	1	1
1	0	1	0	Φ
2	1	0	Φ	0
3	1	1	0	Φ

- We have to write at least 2 of the three different groups (1-generating, 0-gene., don't care)

$$y_1 = f(x_1, x_2) = U_1(0) + U_0(1, 3) \quad \text{there are 2 more repr., but enough}$$

$$y_2 = f(x_1, x_2) = U_3(1, 3) + U_1(0)$$

1st Canonical Form (SOP)

- a function with 2 variables has 4 minterms.

$ab, \bar{a}b, a\bar{b}, \bar{a}\bar{b}$

A	B	C	F	\bar{F}	
0	0	0	0	1	m0
0	0	1	1	0	m1
0	1	0	0	1	m2
0	1	1	1	0	m3
1	0	0	0	1	m4
1	0	1	1	0	m5
1	1	0	1	0	m6
1	1	1	1	0	m7

$$F(A, B, C) = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \xrightarrow{\text{simplify}} AB + C$$

$$\overline{F(A, B, C)} = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

$$F(A, B, C) = \sum m(1, 3, 5, 6, 7)$$

$$F = \sum_{A, B, C} (1, 3, 5, 6, 7)$$

2nd Canonical Form (POS)

- a function with 2 variables has 4 maxterms.

$$a+b, \bar{a}+b, a+\bar{b}, \bar{a}+\bar{b}$$

A	B	C	F	\bar{F}	
0	0	0	0 -	1	M0
0	0	1	1	0 -	M1
0	1	0	0 -	1	M2
0	1	1	1	0 -	M3
1	0	0	0 -	1	M4
1	0	1	1	0 -	M5
1	1	0	1	0 -	M6
1	1	1	1	0 -	M7

$$F(A,B,C) = (A+B+C) \cdot (A+\bar{B}+C) \cdot (\bar{A}+B+C) \xrightarrow{\text{simplify}} (A+C) \cdot (B+C)$$

$$\overline{F(A,B,C)} = (A+B+\bar{C}) \cdot (A+\bar{B}+\bar{C}) \cdot (\bar{A}+B+\bar{C}) \cdot (\bar{A}+\bar{B}+C) \cdot (\bar{A}+\bar{B}+\bar{C})$$

$$F(A,B,C) = \prod M(0,2,4)$$

$$F = \pi_{A,B,C}(0,2,4)$$

Conversions Between Canonical Forms

Complement


$$F(A,B,C) = \sum m(1,3,5,6,7) \rightarrow \overline{F(A,B,C)} = \sum m(0,2,4) \rightarrow \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

↓ De Morgan

$$F(A,B,C) = \prod M(0,2,4) \rightarrow (A+B+C) \cdot (A+\bar{B}+C) \cdot (\bar{A}+B+C)$$

WS

Half Adder →

 


Doesn't contain carry input.

$$s = a \oplus b$$

a, b are 1-bit nums.

$$c = a \cdot b$$

Full Adder →

 


$$s = a \oplus b \oplus c$$

a, b are 1-bit nums.

$$c_{out} = ab + bc + ac$$

Parallel Adder →

 


4-bit PA consist of 4 FA.

A, B are 4-bit nums.

$$\begin{array}{r} A_3 A_2 A_1 A_0 \\ B_3 B_2 B_1 B_0 \\ \hline \text{carry } S_3 S_2 S_1 S_0 \end{array}$$


Parallel Adder (Subtraction) → $A - B$ (4-bit)

$$A - B = A + \bar{B} + 1$$

 


Multiplexer (MUX) (m:1) →

 It selects one input according to selector input.



 
$$\begin{aligned} S=0 &\rightarrow I_0 \\ S=1 &\rightarrow I_1 \\ Z &= \bar{S}I_0 + SI_1 \end{aligned}$$



$$\begin{aligned} S_1=0, S_0=0 &\rightarrow I_0 \\ S_1=0, S_0=1 &\rightarrow I_1 \\ S_1=1, S_0=0 &\rightarrow I_2 \\ S_1=1, S_0=1 &\rightarrow I_3 \end{aligned}$$


Parallel MUX →

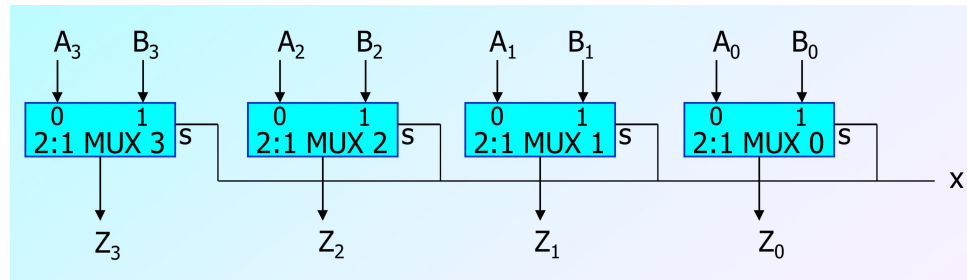


$$\begin{aligned} x=0 &\rightarrow Z=A \\ x=1 &\rightarrow Z=B \end{aligned}$$

Demultiplexer (1:m) →

 It drives the input to the output according to the selector.



 
$$\begin{aligned} S=0 &\rightarrow I=O_0 \\ S=1 &\rightarrow I=O_1 \end{aligned}$$




Decoder →

 Decoder is a demultiplexer with constant 1 input.




n number of selector
 2^n number of output

 We can use decoder as a minterm generator. →
Then implement a function using the minterms.



 If $EN=1$ → outputs are valid.
If $EN=0$ → all outputs are zero.
It creates a new case "three-state outputs"



w6

- PLA \rightarrow input (and) \rightarrow output (or) SOP / AND and OR gates are programmable.
PAL \rightarrow Same structure. / Only AND gates are programmable.

w7

- static 0 hazard \rightarrow POS Form
 - static 1 hazard \rightarrow SOP Form
 - $Z = AB + B'C \rightarrow$ there can be static 1 hazard, to avoid that;
the consensus term of Z should be added to the circuit, but it's not efficient due to the increasing of cost.
- $$Z = AB + B'C + AC$$

w8

- Flip-flop controlled by clock signal. Latch don't.
 - Clock \rightarrow Edge Triggered \rightarrow (Positive logic) $(0 \rightarrow 1) \rightarrow$ rising edge \rightarrow register time = setup t. + hold t.
(negative logic) $(1 \rightarrow 0) \rightarrow$ falling edge
 \rightarrow Input changes in the settling time.
 - A memory unit must have
 - Two stable states
 - Control input
 - S-R Latch
S sets 1 to output when its value 1. R sets 0 to output when its value 1. (S \rightarrow set, R \rightarrow reset)
case 1: $S \rightarrow 1, R \rightarrow 0 \rightarrow Q = 1, Q' = 0$
 $S \rightarrow 0, R \rightarrow 0 \rightarrow Q = 1, Q' = 0$
case 2: $S \rightarrow 0, R \rightarrow 1 \rightarrow Q = 0, Q' = 1$
 $S \rightarrow 0, R \rightarrow 0 \rightarrow Q = 0, Q' = 1$
case 3: $S \rightarrow 1, R \rightarrow 1 \rightarrow Q = 0, Q' = 0 \rightarrow$ invalid
If both inputs are zero, latch preserves its state
- CHARACTERISTIC EQUATION: $Q(t+1) = S + Q(t) \cdot \overline{R} \quad (S \cdot R = 0)$

S-R with Enable \rightarrow It preserves its state when the latch is not enabled.

\overline{S} - \overline{R} Latch \rightarrow Designed with NAND gates. $S \rightarrow (\text{Reset})$, $R \rightarrow (\text{Set})$

D Latch

It is designed to avoid undesirable condition of S-R Latch.

$E=1 \rightarrow D=0 \rightarrow S=0, R=1 \rightarrow Q(t+1)=0$

$D=1 \rightarrow S=1, R=0 \rightarrow Q(t+1)=1$

CHARACTERISTIC EQN: $Q(t+1)=D$

$E=0 \rightarrow D=\emptyset \rightarrow S=0, R=0 \rightarrow Q(t+1)=Q(t)$

- D-Latch can be designed like flip-flop. (It has rising edge and falling edge versions.)

T Flip-Flop (Toggle)

$T=0 \rightarrow Q(t+1)=Q(t)$

$T=1 \rightarrow Q(t+1)=Q'(t)$

CHARACTERISTIC EQN: $Q(t+1)=T \oplus Q(t)$

J-K Flip-Flop

- It is combine of both S-R and T flip-flops.

$\left. \begin{array}{l} J=1, K=0 \\ J=0, K=1 \end{array} \right\} \text{S-R Latch } (S:J, R:K) \rightarrow Q(t+1)=1$
 $\rightarrow Q(t+1)=0$

$\left. \begin{array}{l} J=0, K=0 \\ J=1, K=1 \end{array} \right\} \text{Toggle FF} \rightarrow Q(t+1)=Q(t)$
 $\rightarrow Q(t+1)=Q'(t)$

CHARACTERISTIC EQN: $Q(t+1)=J \cdot \overline{Q(t)} + \overline{K} \cdot Q(t)$

w9

Mealy: Output depends on both current state and input values.

Moore: Output depends only on current state.

Note: Change in input; immediately (propagation delay is considered) changes the output in mealy model because output depends on input values.
; doesn't change the output value if the clock signal is not in the setup time.

Analysis of FF

- Determine F functions that enters ff as an input.
- Find the next state exp. using ff char. eqn. and Fs. (H)
- Create state table using next state exp.
- Determine the exp. of output.
- Construct state table for G.
- Draw state diagram (optional)

W10

How to design clocked synchronous sequential circuits

- Determine the model (Mealy or Moore)
- Determine the states
 - Determine state transitions based on inputs
 - Construct the state transition and output table.
- There are $\lceil \log_2 m \rceil$ flip-flops in the circuit (m: number of states)
- Determine which ff is used.
- Determine the F function enters in ff's.

Transition Tables

S-R

symbol	S	R
0	0	0
α	1	0
β	0	1
1	0	0

J-K

symbol	J	K
0	0	0
α	1	0
β	0	1
1	0	0

D

symbol	D
0	0
α	1
β	0
1	1

T

symbol	T
0	0
α	1
β	1
1	0

All Circuits

